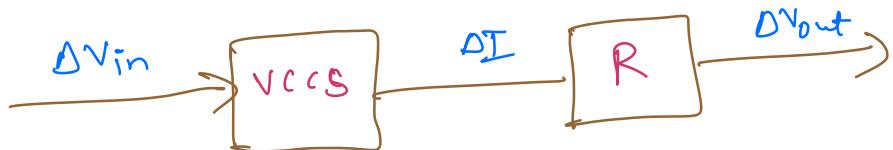


Lecture - 2

Note:-

We skip the derivation of the ' I_s ' saturation current and start from the Amplification stage.


How to Amplify ?




- The VCCS will generate current in response to the voltage variations
- The resistor R converts the current back to voltage domain
- If the product of conversion ratios is larger than '1' then we have a Voltage gain.

$$A_V = \frac{\Delta V_{out}}{\Delta V_{in}}$$

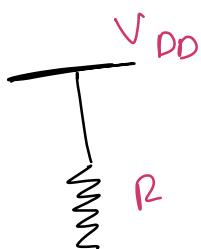Common source amplifier with proper Biasing can act as a "VCCS"



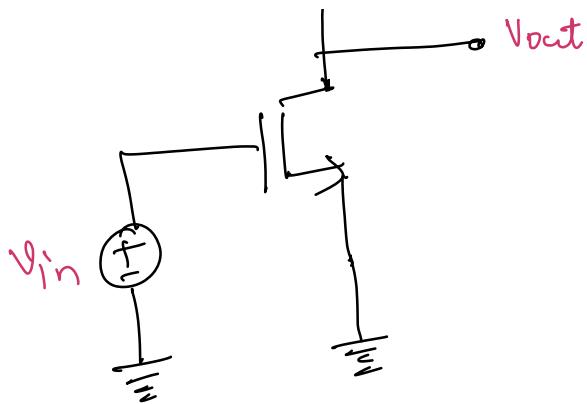

Revanth Reddy
Pannala
EBIT, Unibio
(2020-2022)


Here

$$V_{out} = V_{dd} - I_D R$$

com
 V_{DS}

By varying the input voltage V_{in} we will check the variations in the output voltage.

To do that we will do graphical analysis

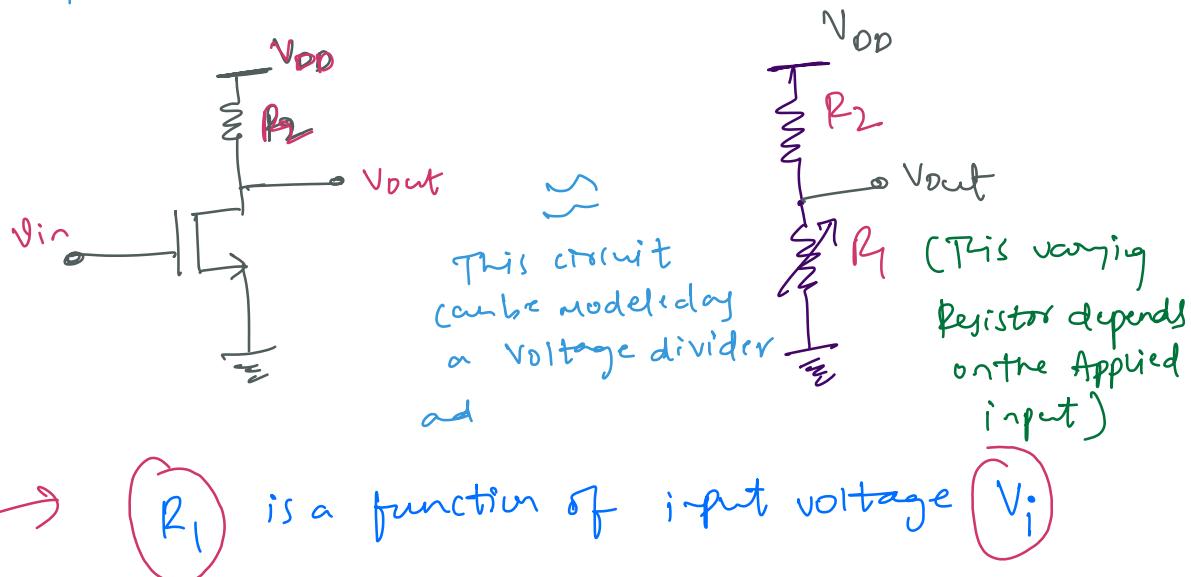


∴ from the voltage divider circuit

⇒

$$V_{out} = \frac{R_1}{R_1 + R_2} V_{DD}$$

from the above equation we can see that

if

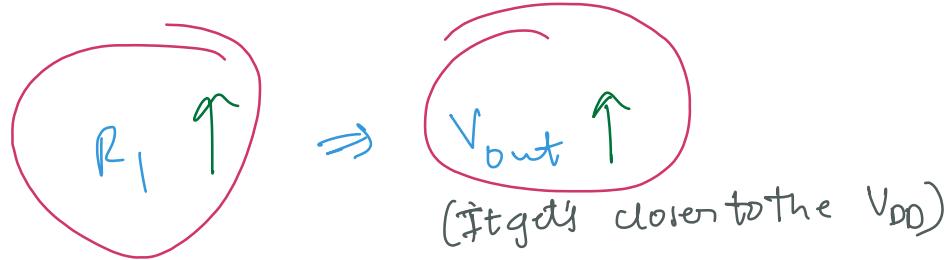

If

$$R_L = \infty \Rightarrow V_{out} = V_{DD}$$

→ now let's try and apply the current formula we derived for Triode Region and Saturation Region for a MOS device

let's look at primary conditions for a Transistor to be ON -

(i) $V_{GS} > V_T \Rightarrow V_{in} > V_T$

Transistor
ON
with well formed
channel


(ii) The device works in Saturation when

$$V_{DS} > V_{GS} - V_T$$

⇒ ∵ for the current circuit above the equation translates to

$$V_{out} \geq V_{in} - V_T$$

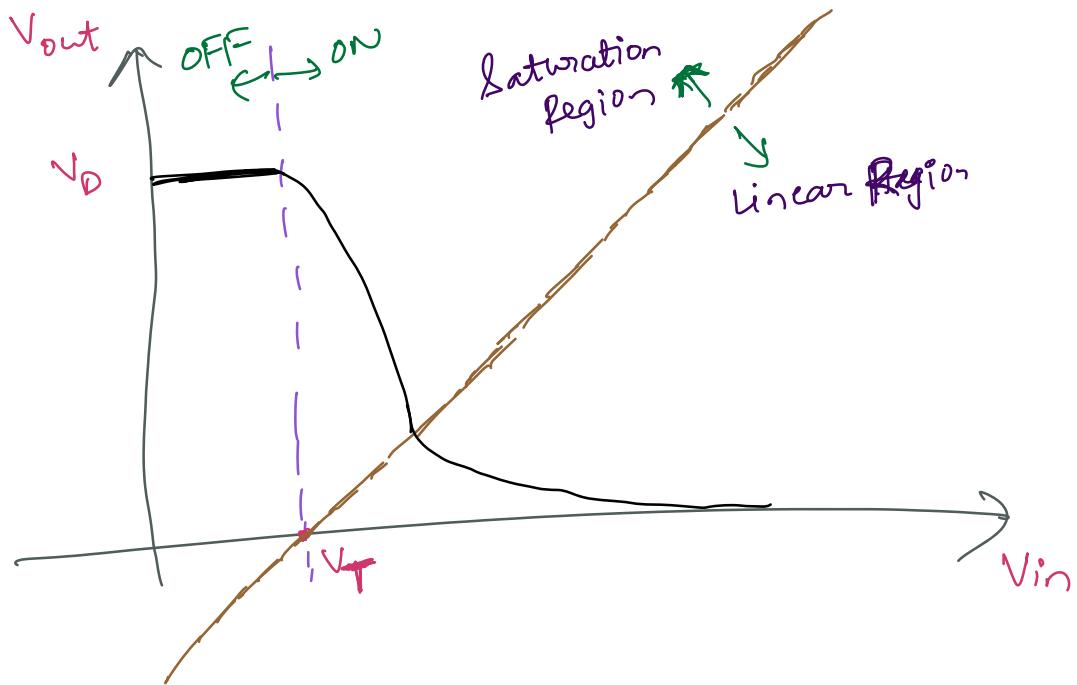This is the equation of line with slope = 1
y intercept = $-V_T$



→ When the Transistor is OFF then The $I_D = 0$
 Then $V_{out} = V_{DD}$
 \therefore In OFF Region $V_{out} = V_{DD}$

→ we know from the above equations that if

$R_L \downarrow$ then $V_{out} \downarrow$

Q Therefore what happens when we increase the value of V_{in} above threshold ?


→ Firstly R_L decreases because The channel size will increase and as V_{in} increases

R_L keeps decreasing.

∴ according to our observation $V_{out} \downarrow$

Q More specifically what happens when we are in Saturation Region?

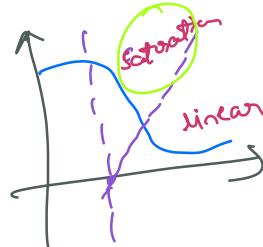→ we have discussed that Saturation current



$$I_D = \frac{1}{2} \mu_n \text{cox} \frac{W}{L} (V_i - V_T)^2 \quad \rightarrow ①$$

$$V_{out} = V_{DD} - R_2 I_D$$

Let $\mu_n \text{cox} \frac{W}{L} = B$ → It is called intrinsic conductivity

$$I_D = \frac{B}{2} (V_i - V_T)^2 \quad \rightarrow ②$$

$$B = \beta' \frac{W}{L}$$

$$I_D = \beta' \frac{W}{L} (V_i - V_T)^2 \quad \rightarrow ③$$

where

$$\beta' = \mu \cdot \text{cox}$$

→ we use either one of the above equations for I_D depending on our convenience.

In LTSPICE
it is referred
to as k_p


β : Technological parameter

w/l : Geometric property which are under designers control.

→ For Linear Region

$$I_D = \beta \left[(V_{GS} - V_T) - \frac{V_{DS}}{2} \right] V_{DS}$$
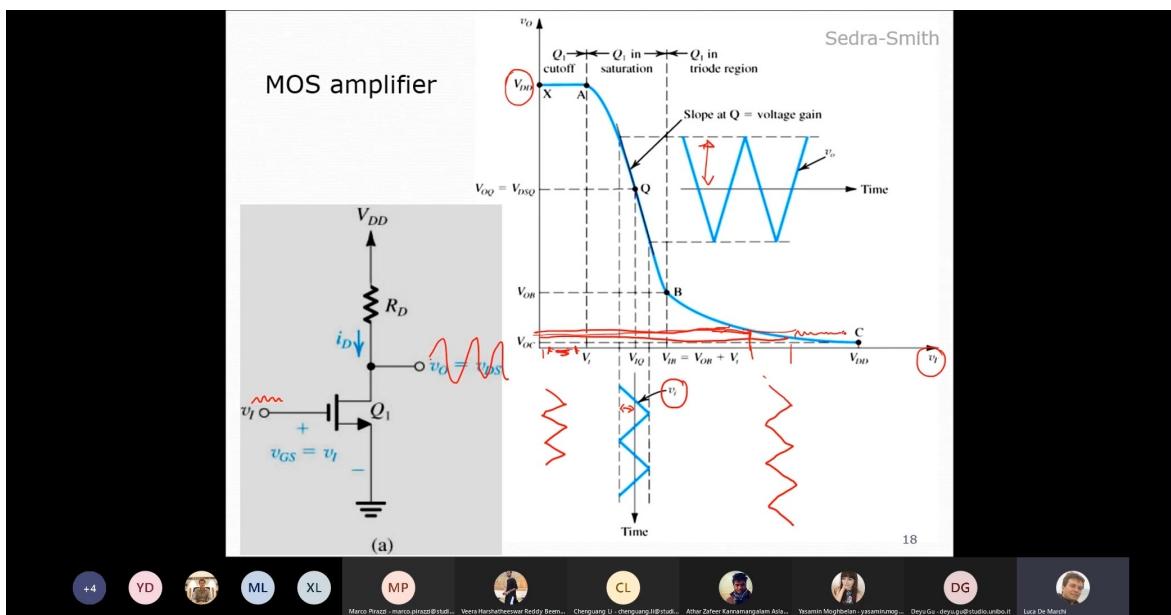
$$\Rightarrow \beta \left(V_{in} - V_T - \frac{V_{out}}{2} \right) V_{out}$$




Note

From the above study and figure it is clear that MOS Transistor can be used as an amplifier but only in Saturation Region.

Graphical Representation of Gain

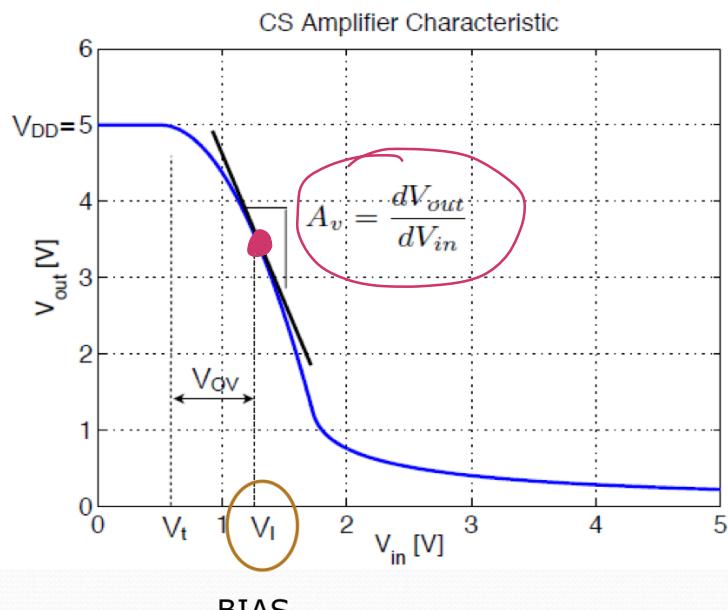- The slope of the tangent to V_{out} - V_{in} characteristic at any given input voltage is the so called "small-signal voltage gain" of the amplifier (A_v) around that point.



M. Hekmat EE114S

2

- even in the Saturation Region the Gain is not same. This Non-linearity is a problem.
- when we have $V_{in} = V_1$ we can approximate the Non-linear behaviour into


1^o
a linear one as indicated by the line -

→ what we want to do is develop a
linear model for an MOS device which
is intrinsically Non-linear.

Q How can we do this ?

We can exploit the Taylor Expansion
concept.

* If we look at the circuit -

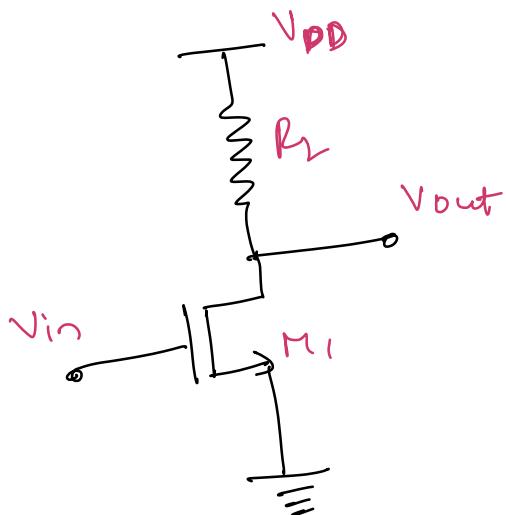

$$I_{R_2} = I_{D1}$$

(current through Resistor R_2
= Saturation current of
the MOSFET M_1)

$$I_{R_2} = I_{D1}$$

$$\Rightarrow \frac{V_{DD} - V_{out}}{R_2} = \frac{\beta}{2} (V_{in} - V_T)^2$$

This is clearly a Non linear Relationship because we have this Quadratic Expression.

→ ∴ we have that

$$V_{out} = f(V_{in})$$

using Taylor's Series Expansion -

If we have an arbitrary function -

$$y = f(x)$$

Then we can define an operating point

(x₀)

Quiescent point

$$y_0 = f(x_0)$$

Then if we move the input from the Quiescent (x₀) operating point to another position we can express this movement as

$$x = x_0 + \Delta x$$

|

This variation in the input also causes

Variation in the o/p. This shall be given by

$$y = y_0 + \Delta y$$

∴ with certain degree of Approximation
we can express.

$$y = y_0 + \Delta y = f(x_0) + f'(x_0) \Delta x$$

↓
Taylor series expansion in
linear term
only

$$\therefore \Delta y \approx f'(x_0) \Delta x$$

This approximation becomes
equality if the variation
are infinitely small.

→ Applying this concept to the Amplifier say

when $V_{out} = f(V_{in})$

$$\Rightarrow \frac{V_{op} - V_{out}}{R_2} = \frac{B}{2} (V_T - V_T)^2$$

$$\Rightarrow V_{out} = V_{DD} - \frac{B}{2} (V_{in} - V_T)^2 \cdot R_2$$

Here $y = V_{out}$, $x = V_{in}$

 Let's calculate the derivative of $y = f(x)$

$$\Rightarrow \frac{dV_{out}}{dV_{in}} = 0 - \frac{B}{2} \cancel{(V_{in} - V_T)} R_2$$

$$\Rightarrow \frac{dV_{out}}{dV_{in}} = -B \cdot R_2 \cdot (V_{in} - V_T)$$

 Gain

$$A_V = \frac{dV_{out}}{dV_{in}} = -M_n C_{ox} \frac{W}{L} R_2 V_{ov}$$

$$V_{ov} = V_{in} - V_T = \text{Overdrive Voltage}$$

 This linearization concept is really pervasive in Analog design analysis. Which we will talk about in Small signal Analysis

→ If we consider small variations close to the operating point. Then we can turn non linear relationship into a linear one with decent approximations -

Fixing an Operating Point \Rightarrow Proper Biasing of the circuit

→ Linearity hugely benefits the analysis of the circuit because we can apply an important tool "Superposition Principle"

i.e.

$$\boxed{f(a+b) = f(a) + f(b)}$$
$$\boxed{f(2a) = 2f(a)}$$

} Benefits of Superposition

Another way to solve the Gain formula

A small additional signal in the active region...

$$V_{out} = V_{DD} - \frac{1}{2}\mu C_{ox} \frac{W}{L} (V_{in} - V_t)^2 \times R$$

$$\begin{aligned} V_{out} + \Delta v_o &= V_{DD} - \frac{1}{2}\mu C_{ox} \frac{W}{L} (V_{OV} + \Delta v_i)^2 \times R \\ \rightarrow \Delta v_o &= -\frac{1}{2}\mu C_{ox} \frac{W}{L} [2V_{OV}\Delta v_i + \Delta v_i^2] \times R \\ &= -\frac{2I_D}{V_{OV}} \Delta v_i \left[1 + \frac{\Delta v_i}{2V_{OV}} \right] \times R \end{aligned}$$

$$\boxed{\Delta v_i \ll V_{OV} \rightarrow \Delta v_o \approx -\frac{2I_D}{V_{OV}} R \Delta v_i}$$

20

Take away message:

If we assume Δv_0 is infinitely small we have:

$$\frac{dV_o}{dV_i} = -\frac{2I_D}{V_{OV}} R = -\mu C_{ox} \frac{W}{L} V_{OV} R = A_v$$

We can have gain ($A_v > 1$) if we choose the parameters properly.

by

Revanth Reddy Pannala
EBIT, Unibio