
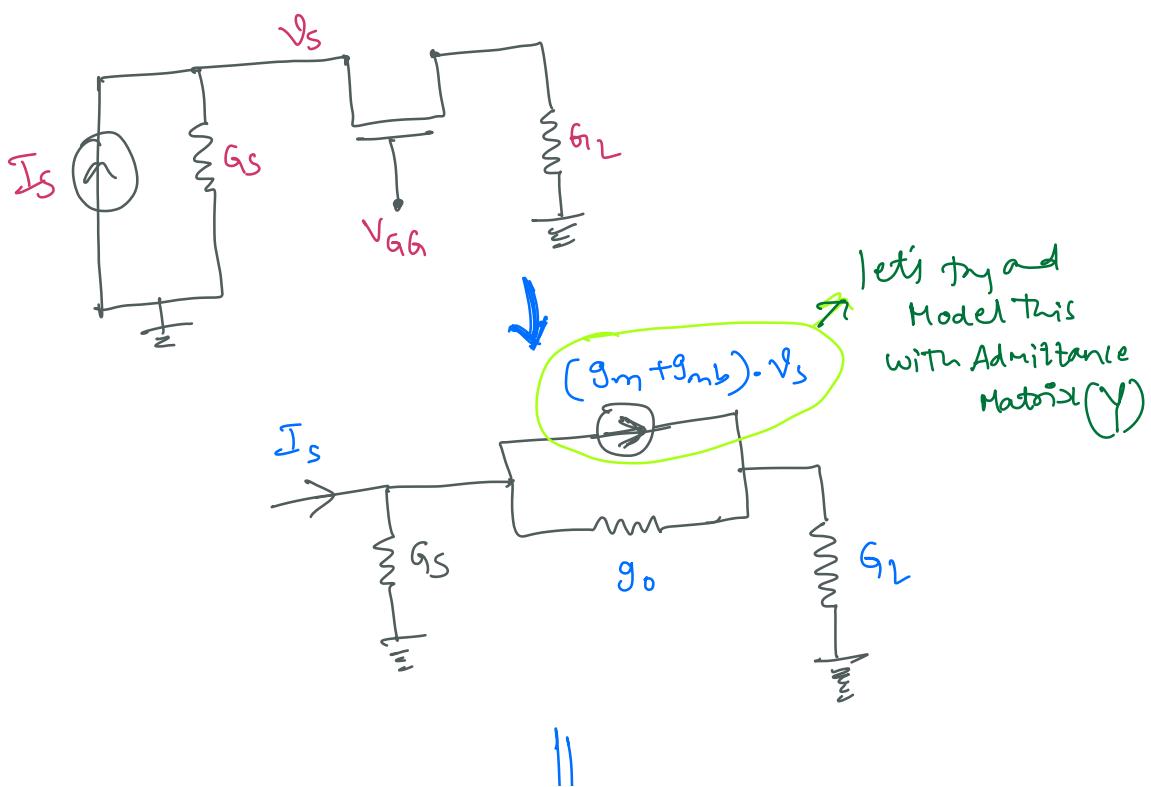



Lecture - 8

Revarth Reddy
Pannala

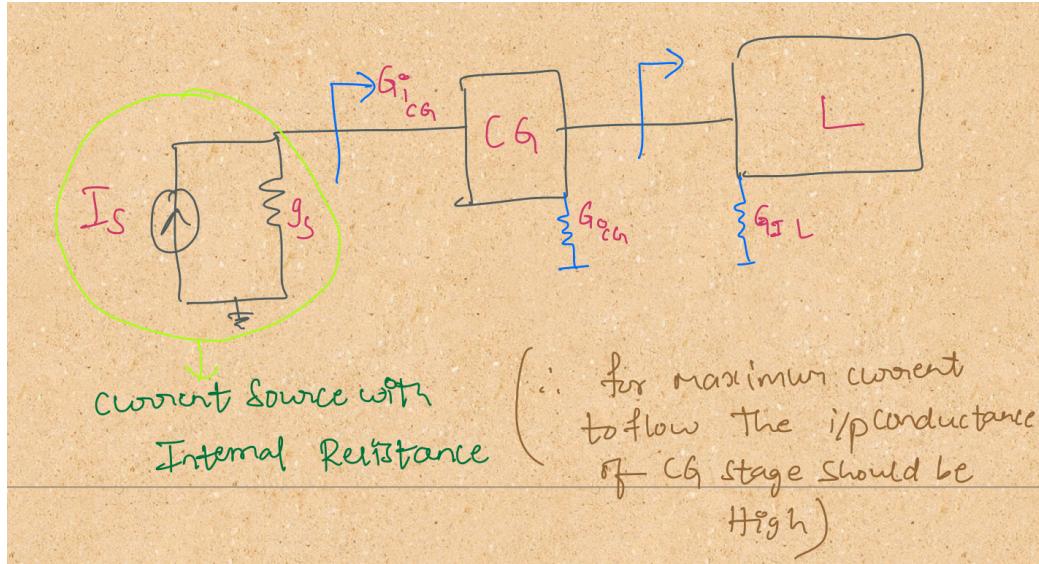

Continuation of Common Gate Stage




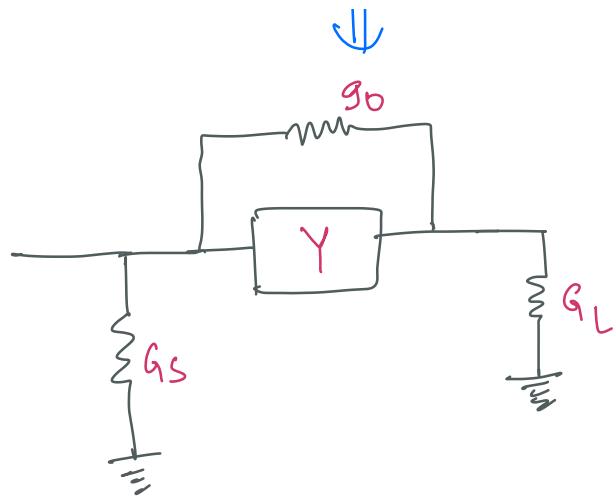

→ For Admittance Matrix (\mathbf{Y})

1)

$$y_{11} = \left. \frac{i_1}{v_1} \right|_{v_2=0} = (g_m + g_{mb}) \triangleq g_m^1$$

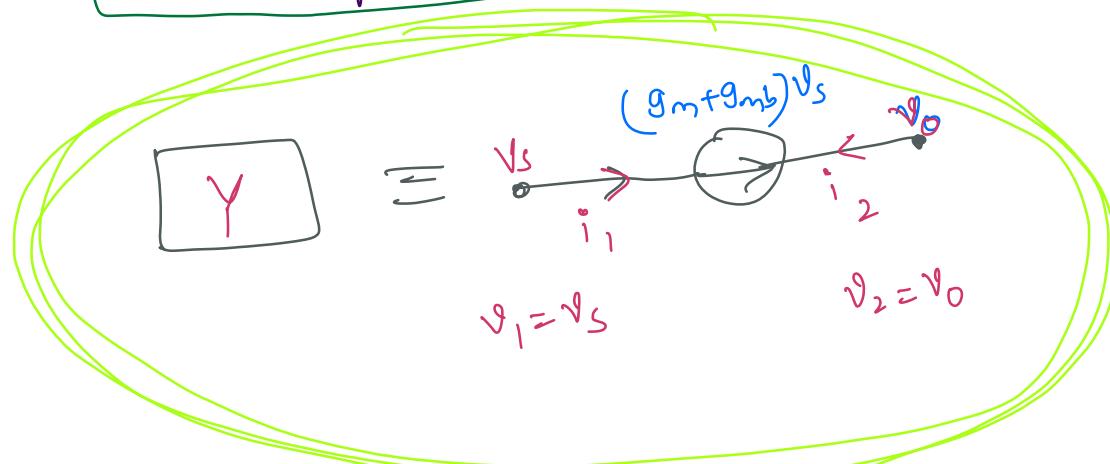

2)

$$y_{21} = \left. \frac{i_1}{v_2} \right|_{v_1=0} = 0$$

$$\begin{aligned} & \because v_1 = v_s \\ & \therefore v_r = 0 \end{aligned} \Rightarrow i_1 = (g_m + g_{mb})v_s = 0$$

-- vs --

3)
$$y_f = \frac{i_2}{v_1} \Big|_{v_2=0} = -g_m^1$$

4)
$$y_o = \frac{i_2}{v_2} \Big|_{v_1=0} = 0$$

→ Now we have the Elements of The admittance Matrix. what we can do is to apply some of the Rules we have derived for circuit parameters calculation.

They are

$$A_V = -\frac{y_f}{y_o} = -\frac{(-g_m^1 - g_o)}{g_o + g_L} = \frac{g_m^1 + g_o}{g_o + g_L} = \frac{G_T}{G_o + G_L}$$


$$Y_i = \frac{\Delta Y}{g_o}$$


$$Y_o = \frac{\Delta Y}{Y_i}$$

Similarly other quantities can be found out.


$$A_i^o = \frac{y_f}{y_i}$$

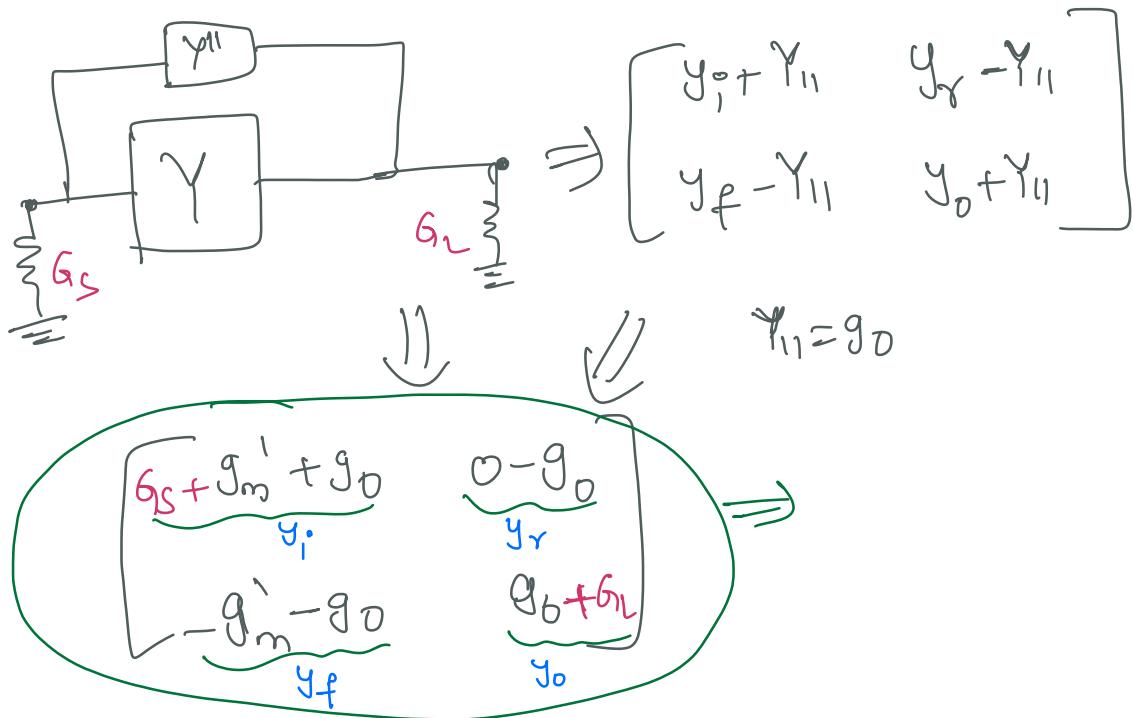→ Before writing the values, we need to update our matrix as the circuit also contains g_D in parallel to γ and g_S & g_L connected to i/p & o/p.



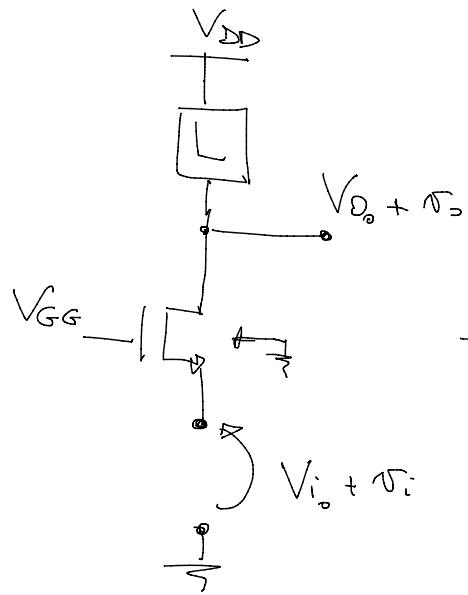

S.S.C.

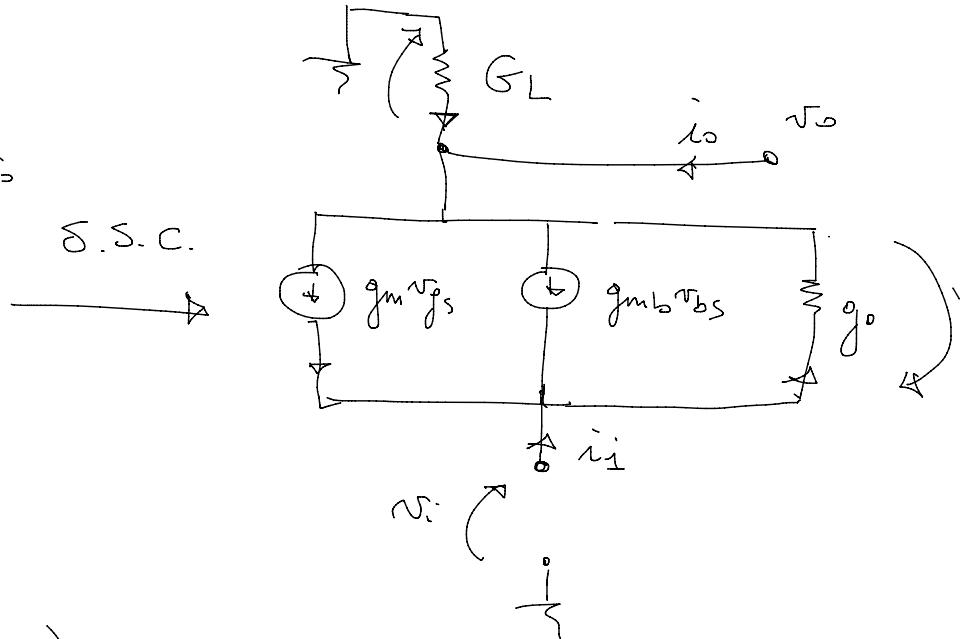

$$G_L \cdot (-v_o) = g_o (v_o - v_i) - g_m v_i - g_{mb} v_i$$



$$v_o (G_L + g_o) = v_i (g_m + g_{mb} + g_o) \underbrace{G_T}_{\Rightarrow \frac{v_o}{v_i} = \frac{G_T}{G_L + g_o}}$$

$$G_I = \frac{i_i}{v_i} \left\{ \begin{array}{l} i_i = g_m v_i + g_{mb} v_i + j_0(v_i - v_o) \\ i_i = G_T v_i - j_0 v_o \\ i_i = G_T v_i - j_0 \frac{v_o}{v_i} v_i = G_T v_i - j_0 A_{CG} v_i \end{array} \right.$$



$$A_{CG} = \frac{G_T}{G_L + j_0}$$

$$\left. \frac{i_i}{v_i} \right|_{v_o=0} = G_I = G_T - j_0 A_{CG} = G_T \left(1 - \frac{j_0}{G_L + j_0} \right)$$
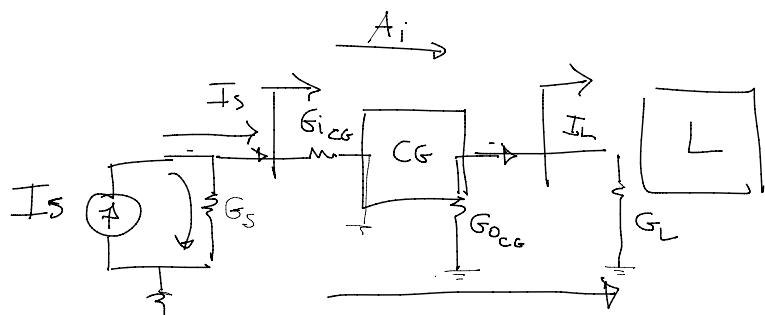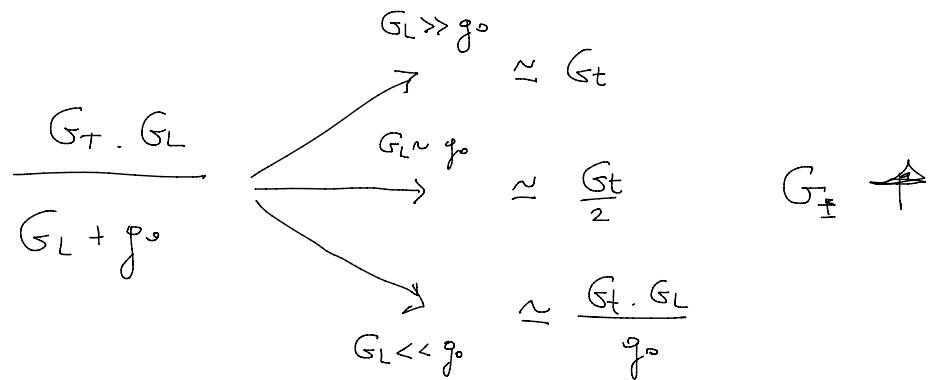
$$G_I = G_T \cdot \frac{G_L + j_0 - j_0}{G_L + j_0} = \frac{G_T \cdot G_L}{G_L + j_0}$$



--- ~ Y

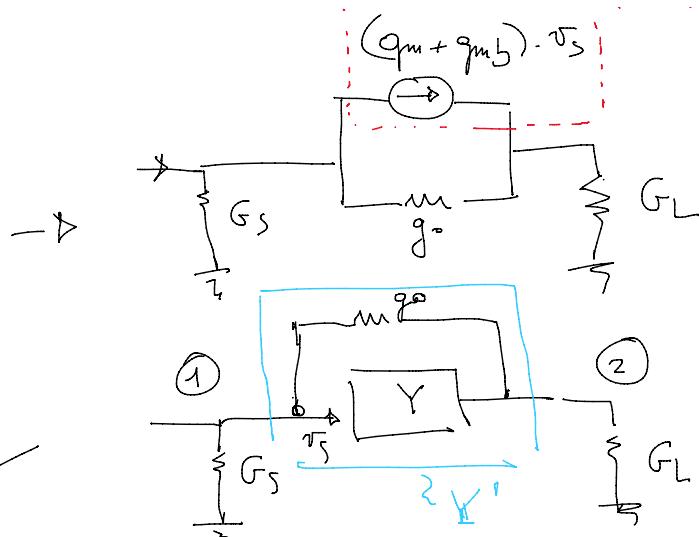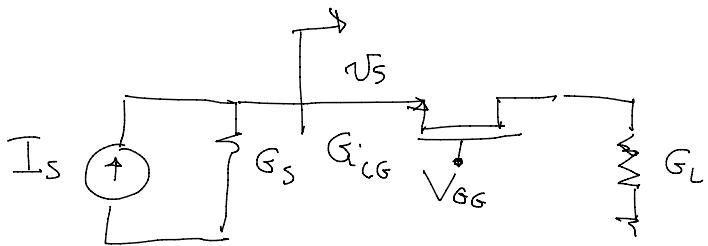


$$y_i = \frac{i_1}{V_1} \Big|_{V_2=0} = (g_m + g_{mb}) \triangleq g_m'$$

$$y_r = \frac{i_1}{V_2} \Big|_{V_1=0} = 0$$

$$y_f = \frac{i_2}{V_1} \Big|_{V_2=0} = -g_m'$$

$$y_o = \frac{i_2}{V_2} \Big|_{V_1=0} = 0$$

→

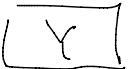

$$(g_m + g_{mb}) V_S$$

$$\sqrt{S}$$

$$i_1$$

$$\sqrt{S}$$

$$V_1$$

$$\sqrt{S}$$


$$V_2$$

$$A_V = -\frac{Y_f}{Y_i}$$

$$Y_i = \frac{\Delta Y}{Y_i}$$

$$Y_o = \frac{\Delta Y}{Y_i}$$

$$A_i = \frac{Y_f}{Y_i}$$

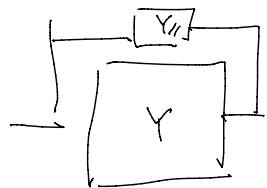

$$\rightarrow \begin{bmatrix} Y_i + Y_L & Y_o - Y_L \\ Y_f - Y_L & Y_o + Y_L \end{bmatrix} \rightarrow \begin{bmatrix} G_S + g_m^i + p_o & -g_o \\ -g_m^i - g_o & +g_o + G_L \end{bmatrix} \sim \begin{bmatrix} Y^1 & \\ & Y^2 \end{bmatrix}$$

$G_S + g_m^i + p_o \quad -g_o$

$+g_o + G_L \quad +g_o$

$Y^1 + G_S + G_L \triangleq Y^2$

(i)

$$A_V = \frac{g_m^i + p_o}{g_o + G_L} = \frac{G_T}{g_o + G_L}$$

(ii)

$$Y_i = \frac{(G_S + g_m^i + p_o)(g_o + G_L) - g_o(g_m^i + p_o)}{g_o + G_L} =$$

$$= \frac{G_S(g_o + G_L) + g_m^i g_o + p_m^i G_L + p_o^2 + p_o G_L - g_o g_m^i - g_o^2}{g_o + G_L}$$

$$= G_S + \frac{g_m^i G_L + p_o G_L}{g_o + G_L}$$

1

Y_i

$$\left[\begin{array}{c} 0 \\ Y_{i,CG} \end{array} \right]$$

$$Y_{i,CG} = \frac{G_L \cdot G_T}{g_o + G_L} = \frac{G_T}{g_o \cdot R_L + 1}$$

$$R_L = \frac{1}{G_L}$$

$$g_o R_L \gg 1$$

$$Y_{i,CG} \approx g_o^{-1}$$

$$Y_{i,CG} \approx \frac{G_T}{g_o \cdot R_L} \approx \frac{q_m}{g_o \cdot R_L} \sim 100$$

$$R_{i,CG} \approx \frac{R_L}{100}$$

(iii)

$$Y_o'' = \frac{\Delta Y''}{y_i^n} = \frac{G_L \cdot G_T + G_S (j_0 + G_L)}{q_m^i + j_0 + G_S} =$$

$\underbrace{q_m^i + j_0 + G_S}_{G_T}$

$$\frac{G_L (G_T + G_S) + G_S j_0}{G_T + G_S} = G_L + \frac{G_S j_0}{G_T + G_S}$$

$$\frac{1}{j_0} \triangleq R_{ds}$$

$$Y_{O_{CG}} = \frac{G_S \cdot j_0}{G_T + G_S} \rightarrow R_{O_{CG}} = \frac{G_T + G_S}{G_S \cdot j_0} = \frac{1}{j_0} + \frac{1}{j_0} \frac{G_T}{G_S} = \frac{1}{j_0} \left(1 + \frac{G_T}{G_S} \right) = \boxed{\frac{1}{j_0} \left(1 + G_T \cdot R_{ds} \right)}$$

R_o


(iv)


$$A_i = \frac{y_F}{y_i} \quad \left| \begin{array}{l} \\ \\ G_S = 0 \end{array} \right. = \frac{i_e}{i_A} \Rightarrow - \frac{j_0 + q_m^i}{q_m^i + j_0} = -1$$

$$\frac{i_2}{i_1} = -1$$

(8)

$$i_0 = -i_2$$

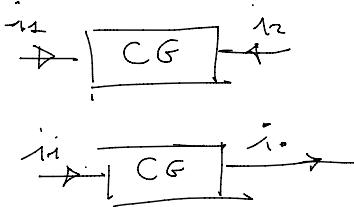


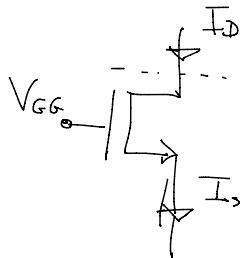


$$\left[\frac{i_o}{i_i} = 1 \right]$$

Current Gain
is Unity

$$\frac{i_o}{i_i} = 1$$

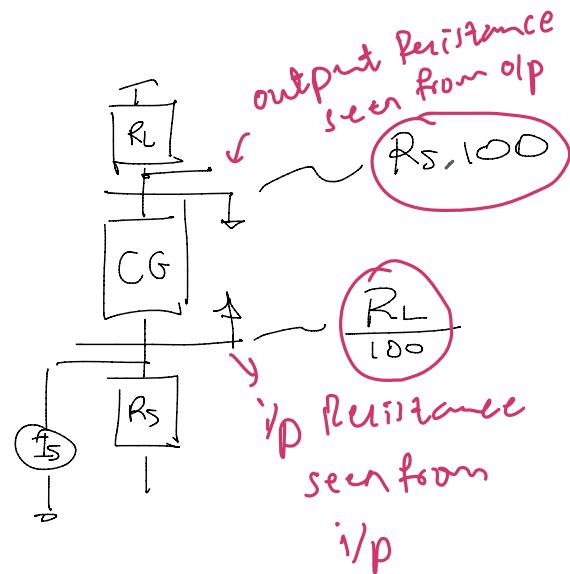


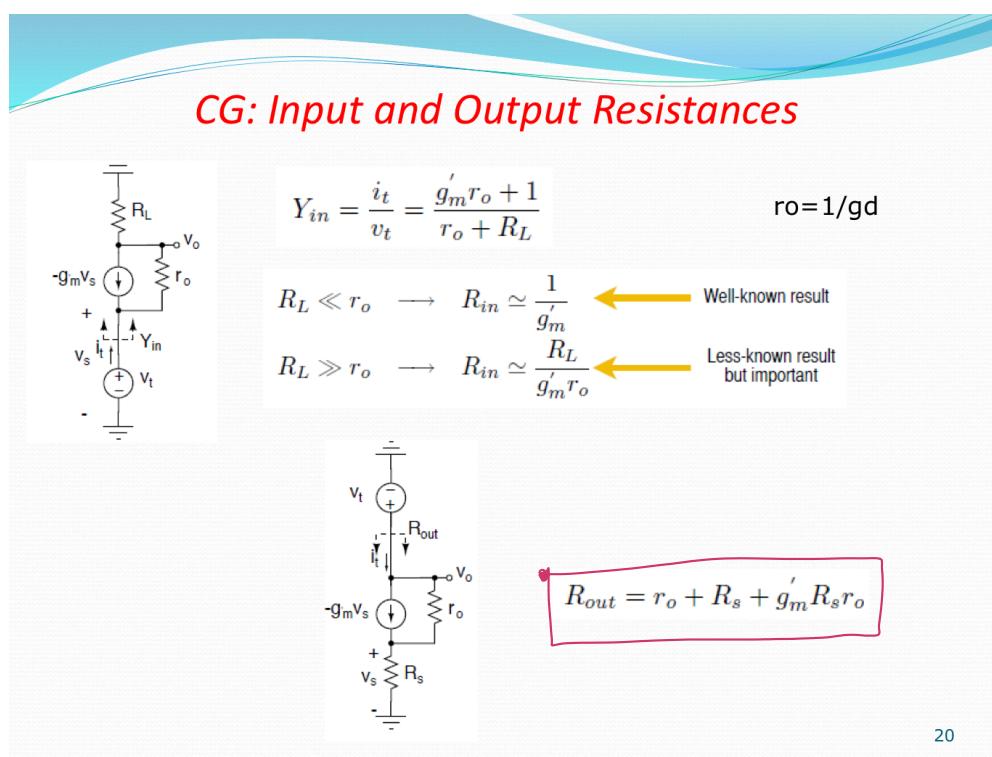

Application of CG stage in Transmission lines

Transmission lines (I)

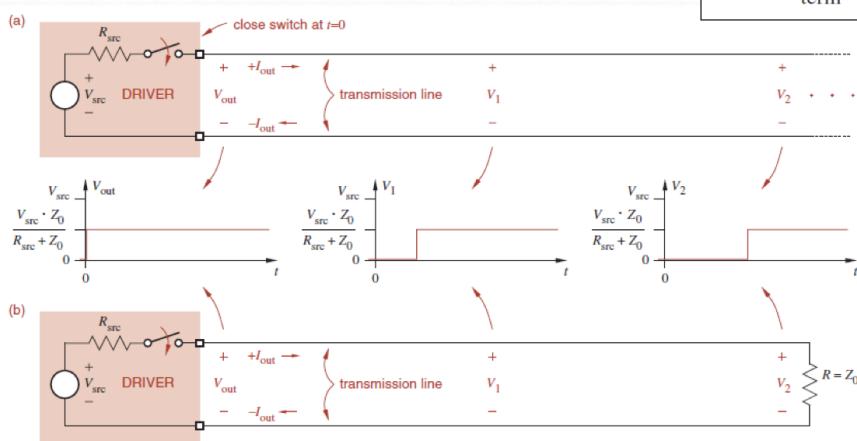
$$\rho = \frac{Z_{\text{term}} - Z_0}{Z_{\text{term}} + Z_0}$$



Transmission lines: (a) with infinite length; (b) with finite length, terminated with characteristic impedance.



Transmission lines (II)

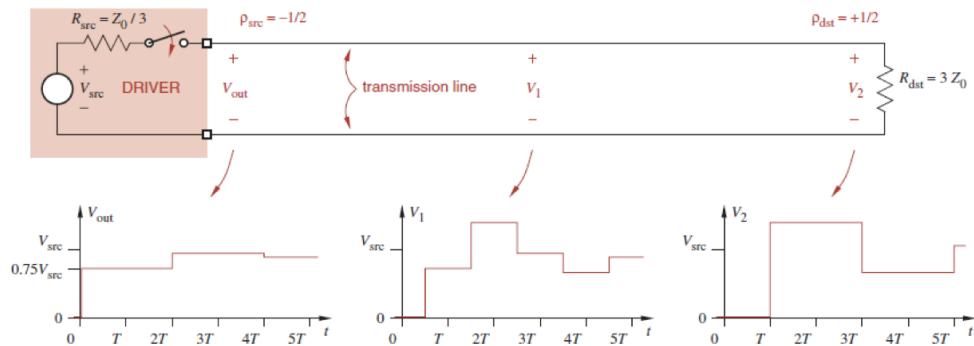



A transmission line that is not matched at either end

Digital Design Principles and Practices, Fourth Edition, by John F. Wakerly

22



Intuitive Analysis of CG

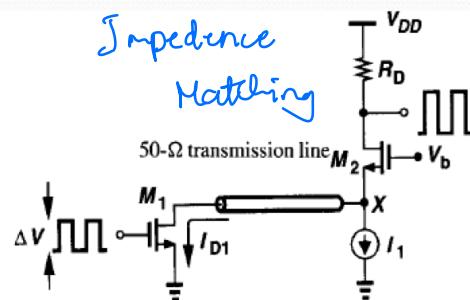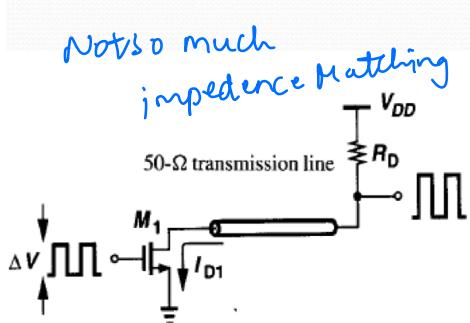

$$1/(g_m + g_{mb}) = 50 \Omega$$




RZ

23



MOSFET Elementary Stages: Summary

- Common source
 - VCCS.
 - A good voltage amplifier when terminated with a large impedance.
- Common gate
 - Typically low input impedance, high output impedance.
 - Can be used to improve the intrinsic voltage gain of a common source stage:
 - "Cascode" stage
- Common drain
 - Typically high input impedance, low output impedance.
 - Great for shifting the DC operating point of signals.
 - Useful as a voltage buffer when swing and nonlinearity are not an issue.

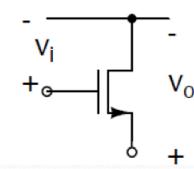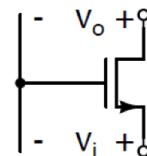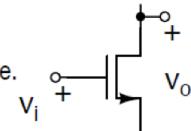


24



Cascade Configuration

Widely Used Two-transistor Circuits

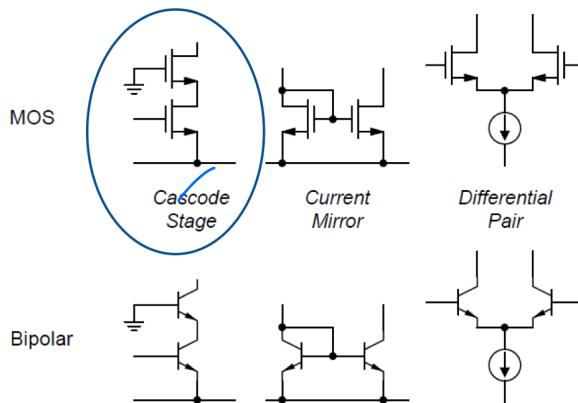

25

Outline



- CMOS cascode diagram
- Small-signal
- The stage as a CS+CG cascade
- Avo
- Transfer charact at the two output nodes



MOSFET Cascode

$$A_V \approx g_{m1} \{ [r_{o1} r_{o2} (g_{m2} + g_{mb2})] \parallel R_D \}$$
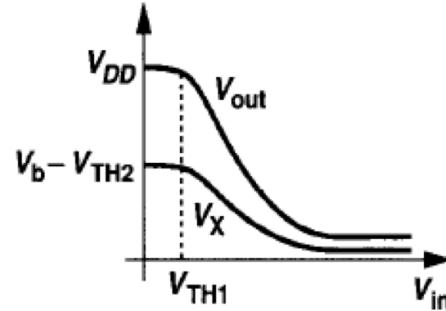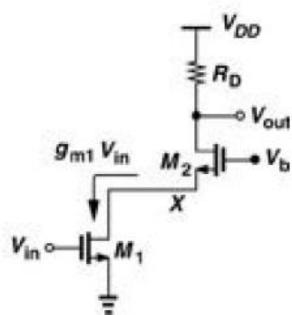
$$\begin{aligned} Rout &= \{ [1 + (g_{m2} + g_{mb2}) r_{o2}] r_{o1} + r_{o2} \} \parallel R_D \\ &\approx [r_{o1} r_{o2} (g_{m2} + g_{mb2})] \parallel R_D \end{aligned}$$



27

By
Revanth Reddy Pannala
EBIT, UnibO