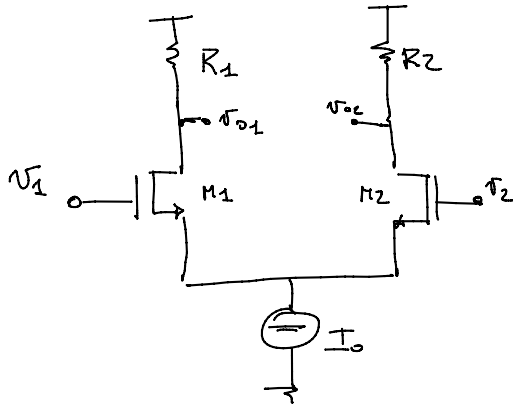


lecture-12



Revanth Reddy
Pannala
EBIT, Unibo



$$v_1 \neq -v_2$$

$$\begin{cases} v_d = v_1 - v_2 \\ v_c = \frac{v_1 + v_2}{2} \end{cases}$$

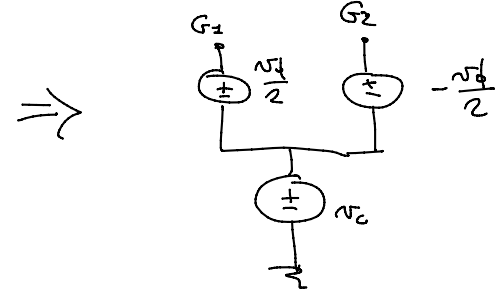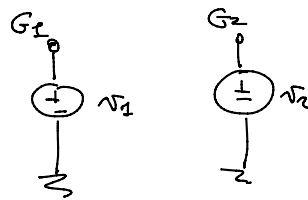
$$\Rightarrow \begin{cases} v_1 = v_c + \frac{v_d}{2} \\ v_2 = v_c - \frac{v_d}{2} \end{cases}$$





$$v_c = 0 \Rightarrow \begin{cases} v_1 = \frac{v_d}{2} \triangleq \delta \\ v_2 = -\frac{v_d}{2} \triangleq -\delta \end{cases}$$

$$v_c \neq 0 \quad v_d = 0$$
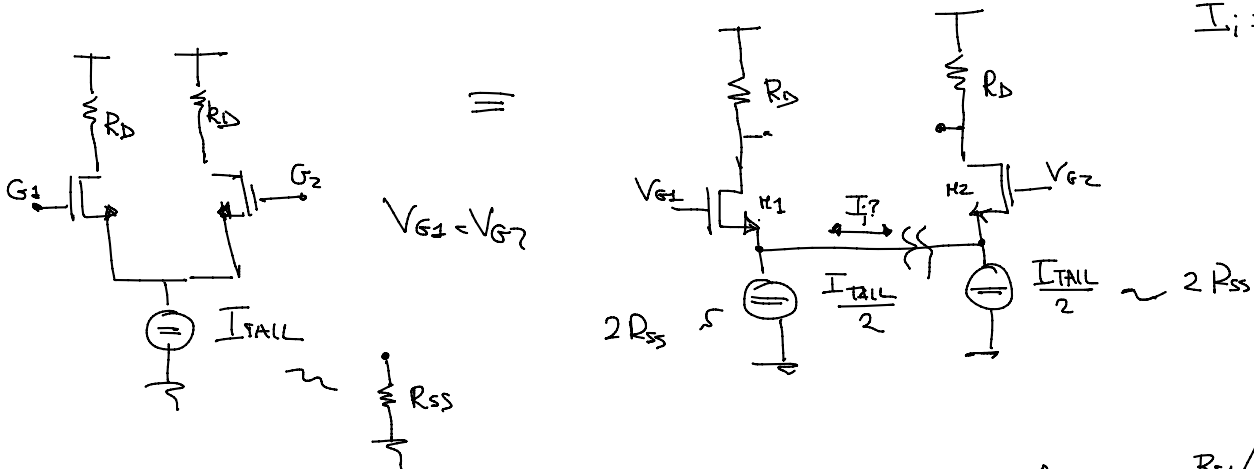
$$\left. \begin{aligned} R_1 &= R_2 \triangleq R_D \\ S_1 &= S_2 \end{aligned} \right\} \Rightarrow \begin{aligned} I_{d1}, I_{d2} &= I \\ i_1 &= i_2 \end{aligned}$$



$$I_i = 0$$

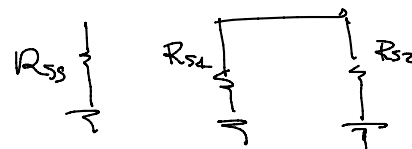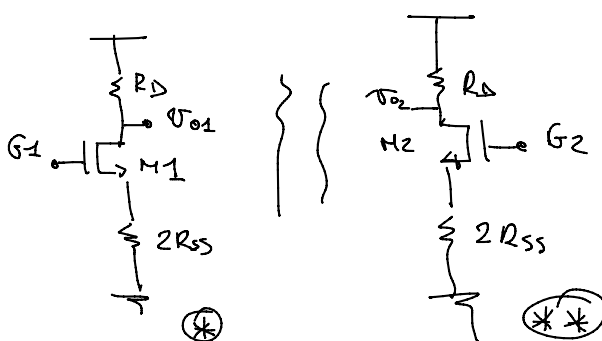

$$R_{S1} // R_{S2} = R_{SS}$$

$$\frac{R_{S1} \cdot R_{S2}}{R_{S1} + R_{S2}} = R_{SS}$$

$$\frac{R_{S1}'}{2 R_{S1}} = R_{SS}$$

$$R_{S1} = R_{S2} = 2 R_{SS}$$

$$(*) = (*) (*) = \text{Double load}$$

$$v_{G1} = v_{G2} = v_c$$

$$G_S = \frac{1}{2R_{SS}}$$

$$\left. \frac{v_{o1}}{v_c} = \frac{v_{o2}}{v_c} = \frac{v_o}{v_i} \right|_{D.L.} =$$

$$= - \frac{g_m}{G_D + g_o + \frac{G_T \cdot G_D}{G_S}}$$

$$G_D = \frac{1}{R_D}$$

$$= - \frac{g_m}{\frac{1}{R_D} + g_o + \frac{G_T \cdot 2R_{SS}}{R_D}} \approx - \frac{g_m R_D}{1 + \underbrace{R_D \cdot g_o}_{\approx 0} + \underbrace{2g_m R_{SS}}_{\text{LARGE}}} = \frac{v_{o1}}{v_c} = A_{CM}$$

$$v_1 = \frac{v_o}{2} = \delta$$

$$v_2 = -\frac{v_o}{2} = -\delta$$

$$v_x = v_1 = 0$$

$$v_{o1} = - \frac{g_{m1}}{g_{o1} + G_{L1}} \cdot \delta$$

$$v_{o2} = - \frac{g_{m2}}{g_{o2} + G_L} \cdot (-\delta)$$

$$G_{L1} = G_D = \frac{1}{R_D} = G_{L2}$$


$$V_{G10} = V_{G20} \Rightarrow \begin{cases} g_{o1} = g_{o2} \triangleq g_o \\ g_{m1} = g_{m2} \triangleq g_m \end{cases}$$

$$v_1 - v_2 = v_{id} = 2\delta$$

$$\frac{v_{o1} - v_{o2}}{v_{id}} = - \frac{g_m}{g_o + G_D} \cdot \frac{(2\delta)}{2\delta} = A_d$$

$$\underline{\underline{A_d}} \gg \underline{\underline{A_{CM}}}$$

$$v_c \neq 0$$

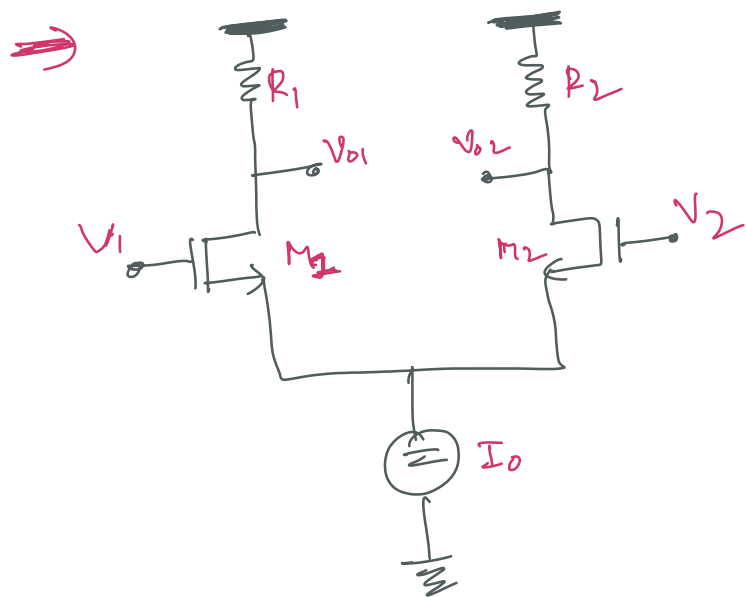

→ $(V_1 \text{ can be different from } -V_2)$ as we have seen in Lecture-11


To take into account all the possible instances we can take all the ^{two} input voltages as the combination of "Common Mode part" and "Differential part."

$$\left. \begin{aligned} V_d &= V_1 - V_2 \\ V_c &= \frac{V_1 + V_2}{2} \end{aligned} \right\} \Rightarrow \begin{aligned} V_1 &= V_c + \frac{V_d}{2} \\ V_2 &= V_c - \frac{V_d}{2} \end{aligned}$$

There can be
Transformed into
Basic circuit equivalents



11- 2 2

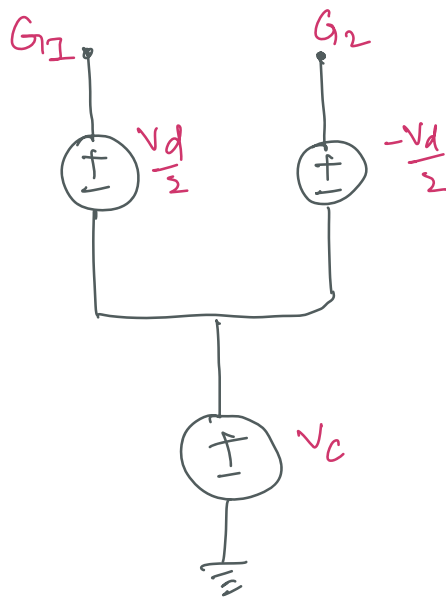

more G_1, G_2
are Gates of Transistor
1 & 2.

→ we have already analyzed system where
Case-1 $V_c = 0$

i.e. $V_1 = \frac{V_d}{2}, V_2 = -\frac{V_d}{2}$

i.e. $V_1 = 8, V_2 = -8$

→ So, we went through the analysis of the above condition in Lecture-12.

→ What we are gonna do now is to study the opposite situation.

Case 2 $V_c \neq 0$ & $V_d = 0$


If we study the Differential pair in

Small signal world where circuit is linear
 Using superposition principle we can
 combine two cases (case 1 & case 2)
 we can fully characterize the operation
of Differential Amplifier.

→ In order to simplify Analysis make

$$R_1 = R_2 \triangleq R_D \quad \left\{ \begin{array}{l} I_1, I_2 = I \\ I_1 = I_2 \end{array} \right.$$


$S_1 = S_2$
 (Source voltages are same)

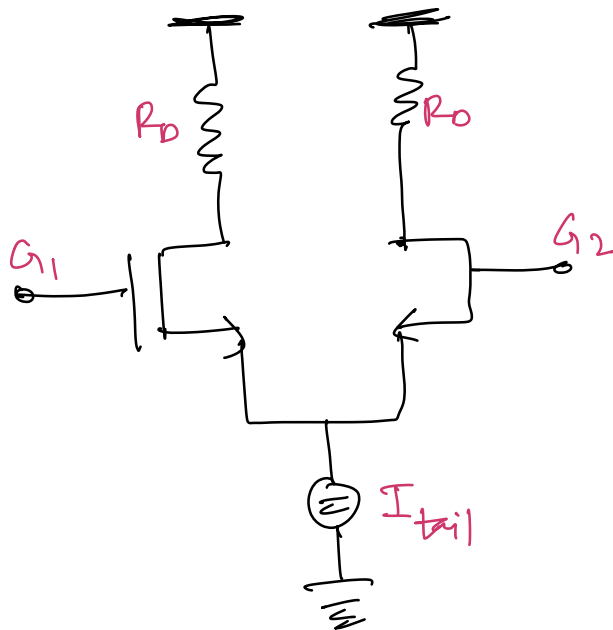

$V_{G1} = V_{G2}$
 $V_{S1} = V_{S2}$
 Then the overdrive
 voltage is also
 same for M_1 & M_2

So this circuit can be redrawn as



||

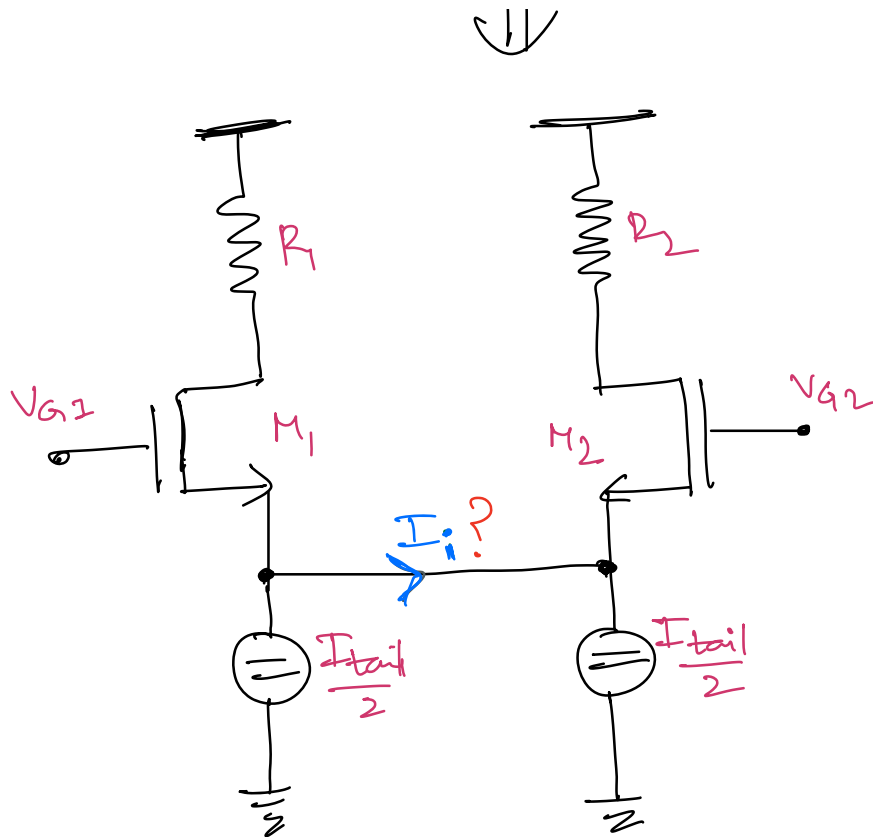

ಶ್ರೀಮತಿ ಬಿ
ಎಸ್.ಎಲ್
EBIT, Unibo

Q What would be the value of current I_i ?

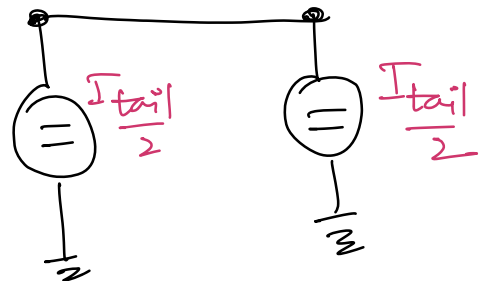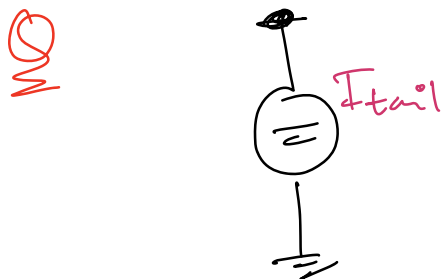By observation since both branches of the circuit are balanced, we can make a preliminary conclusion that $I_i = 0$



The Ideal current always does have a characteristic
 o/p Resistance associated with it -

So, if R_{SS} is the Ideal Characteristic resistance of the I_{tail}

Q What are the characteristic Resistance of two Ideal current sources with currents $\frac{I_{tail}}{2}$?





we should $R_{S1} || R_{S2} = R_{SS}$

$$\Rightarrow \frac{R_{S1} \cdot R_{S2}}{R_{S1} + R_{S2}} = R_{SS}$$

let $R_{S1} = R_{S2}$

$$\Rightarrow \frac{R_{S1}^2}{2 R_{S1}} = R_{SS}$$

$$\Rightarrow R_{S1} = 2 R_{SS}$$

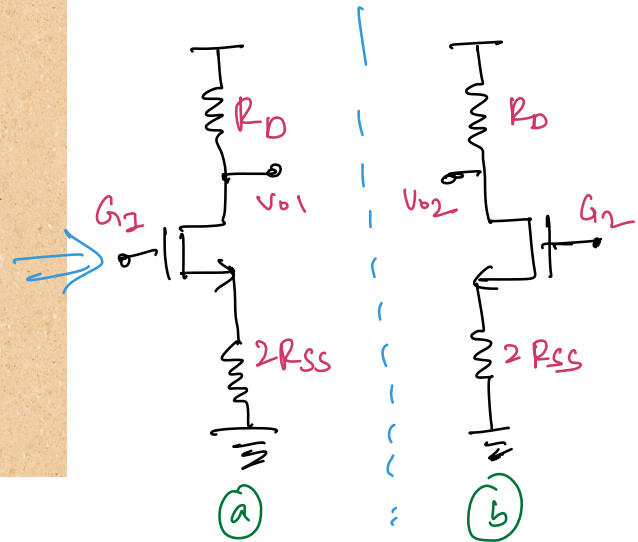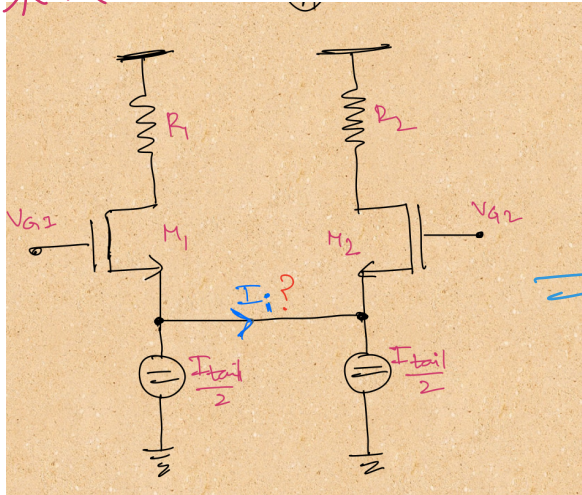

Since $I_i = 0$ we
cancel the circuit

→ What are we interested to determine is
the relationship b/w voltage applied to
Gate and o/p V_{O1} & V_{O2}

$$V_{G1} = V_{G2} = V_C \text{ (common Mode Voltage)}$$


→ Above we can see two "Double loaded
Circuits" after being split as $I_i = 0$

As we have already seen Double loaded

circuits in lecture-10

$$\therefore \left. \frac{V_o}{V_i} \right|_{DL} = \frac{-g_m}{G_D + g_o + G_T \left(\frac{G_D}{G_S} \right)}$$

(Double load configuration)

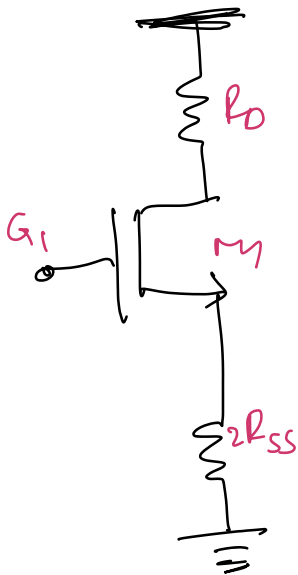

Here $G_S = \frac{1}{2R_{SS}}$

$$G_D = \frac{1}{R_D}$$

జానక రెడ్డి పాండే
EBIT, Unibo

$$\therefore \frac{V_{o1}}{V_c} = \frac{V_{o2}}{V_c} = \left. \frac{V_o}{V_i} \right|_{DL} = \frac{-g_m}{G_D + g_o + G_T \left(\frac{G_D}{G_S} \right)}$$

$$\Rightarrow \frac{-g_m}{\frac{1}{R_D} + g_o + G_T \left(\frac{2R_{SS}}{R_D} \right)}$$

$$\Rightarrow \frac{-g_m R_D}{1 + g_o R_D + g_T \cdot 2R_{SS}} \quad g_T \approx g_m$$

CMG $\Rightarrow$ $\boxed{\frac{-g_m R_D}{1 + g_o R_D + g_m \cdot 2R_{SS}}}$ Common mode Gain.

A_C $\Downarrow$

$$\Rightarrow \boxed{\frac{-g_m R_D}{1 + 2g_m R_{SS}}} \quad \text{Common Mode Gain}$$

when

$$V_1 = \frac{V_d}{2} = f, \quad V_2 = -\frac{V_d}{2} = -f$$

$$\boxed{V_{O1} = \frac{-g_{m1}}{g_{o1} + G_{L1}} \cdot f}, \quad \boxed{V_{O2} = \frac{-g_{m2}(-f)}{g_{o2} + G_{L2}}}$$

In this case $V_{S1} = V_{S2} = 0$

$\therefore$ Differential pair turns out to be combination of two common source stages.

$$G_{L1} = G_D = \frac{1}{R_n} = G_{L2}$$

→ If the nominal Gate conditions

$$V_{G10} = V_{G20} \Rightarrow \begin{cases} g_{o1} = g_{o2} \\ g_{m1} = g_{m2} \end{cases}$$

Then we can conclude that small signal parameters are also equal.

→ This means we can simplify the formula.
for V_{o1} & V_{o2}

we have

$$V_1 - V_2 = V_{id}$$

$$\Rightarrow V_{id} = 8 - (-8) = 28$$

If we compute the differential o/p w.r to
to the differential input.

$$\frac{V_{o1} - V_{o2}}{V_{id}} = \frac{-g_m}{g_o + g_{D1}} \quad \frac{28}{28}$$

Differential Gain

$$\Rightarrow \frac{V_{o1} - V_{o2}}{V_{id}} = \frac{-g_m}{g_o + g_{D1}} = A_d$$

Differential
Gain

This is what is called Differential gain

→ In this expressions we are very much interested in "very large Differential Gain than common mode Gain"

$$A_d \gg A_{cm}$$

Q How can we achieve $A_d \gg A_{cm}$?

we can play with expressions

$$A_{cm} = \frac{-g_m R_D}{1 + g_o R_D + 2g_m R_{SS}} = \frac{V_{oc}}{V_c}$$

$$A_d = \frac{-g_m}{g_o + G_D} \Rightarrow -g_m R_D$$

if g_o is neglected

∴ we can make A_{cm} very less compared

to (A_d) by making (g_{mPSS}) as large as possible.

Differential Circuits: CMRR

This is the part that really carries information

$$v_{id} = v_{i1} - v_{i2}$$

$$v_{ic} = \frac{v_{i1} + v_{i2}}{2}$$



$$v_{od} = v_{o1} - v_{o2}$$

$$v_{oc} = \frac{v_{o1} + v_{o2}}{2}$$

$$v_{o1} = v_{oc} + \frac{v_{od}}{2}$$

$$v_{o2} = v_{oc} - \frac{v_{od}}{2}$$

This is not useful part.

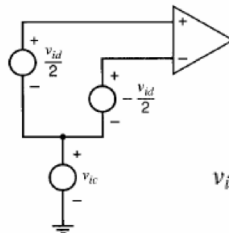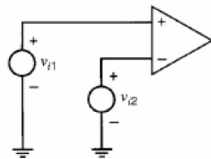

$$v_{i1} = v_{ic} + \frac{v_{id}}{2}$$

$$v_{i2} = v_{ic} - \frac{v_{id}}{2}$$


$$CMRR = \left| \frac{A_{dm}}{A_{cm}} \right|$$

Ratio of Differential part to Common Mode part


GM

46

Differential-Mode Half-Circuit

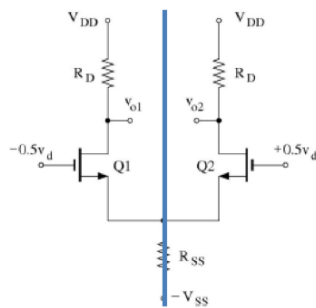

Differential Mode circuit

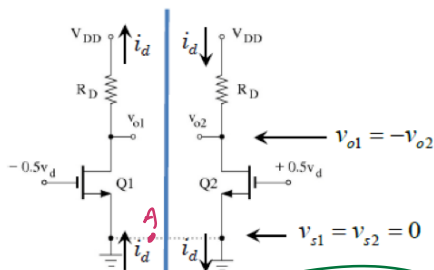

$$v_{s1} = v_{s2} = 0$$

A: virtual Ground


Differential Mode Half-circuit

1. Currents about the symmetry line are equal in value and opposite in sign.
2. Voltages about the symmetry line are equal in value and opposite in sign.
3. Voltage at the symmetry line is zero at Node 'A'.

47



Common-Mode Half-Circuit

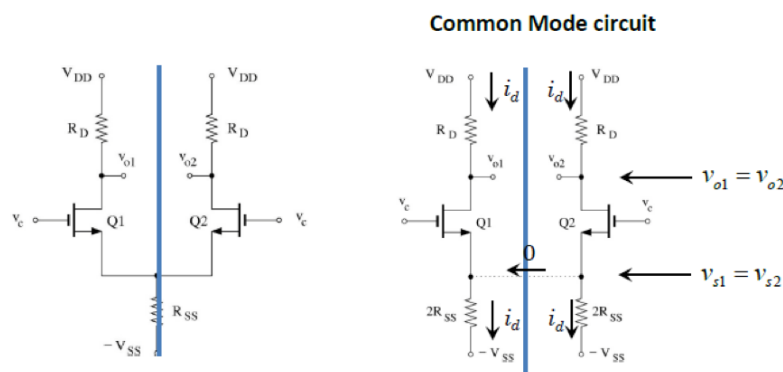

Common Mode Half-circuit


1. Currents about symmetry line are equal.
2. Voltages about the symmetry line are equal (e.g., $v_{o1} = v_{o2}$)
3. No current crosses the symmetry line.

48




Concept of Half-Circuit

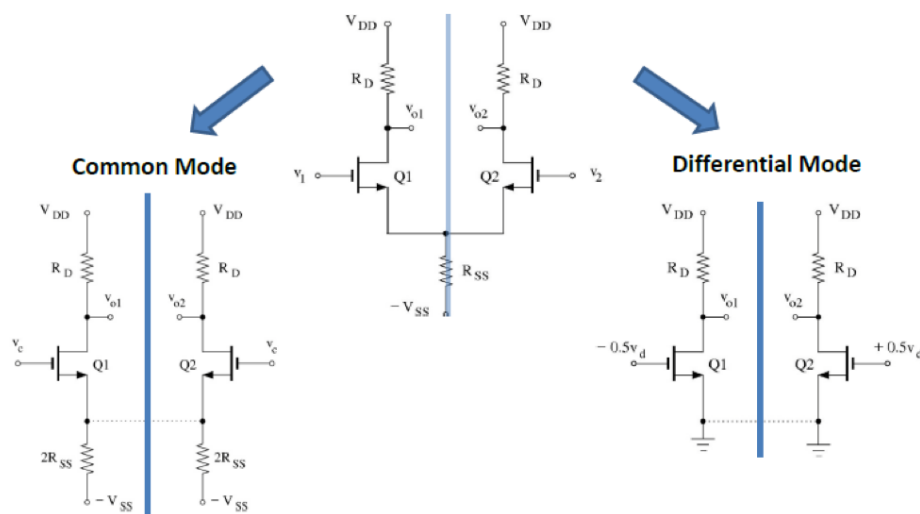- For a symmetric circuit, differential- and common-mode analysis can be performed using "half-circuits."



49

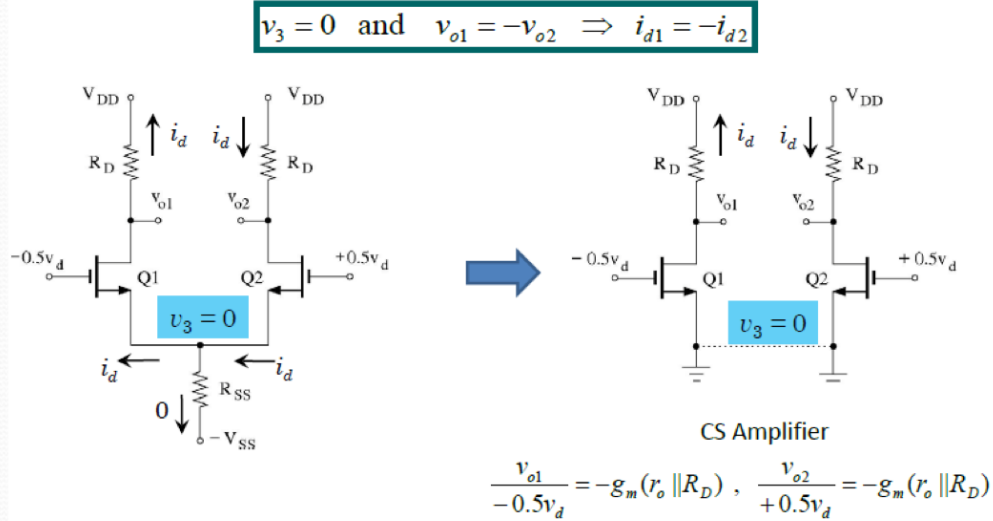
Differential Amplifier- Differential Mode



- Because of the symmetry, the differential-mode circuit also breaks into two identical half-circuits.

Differential Amplifier- Common Mode

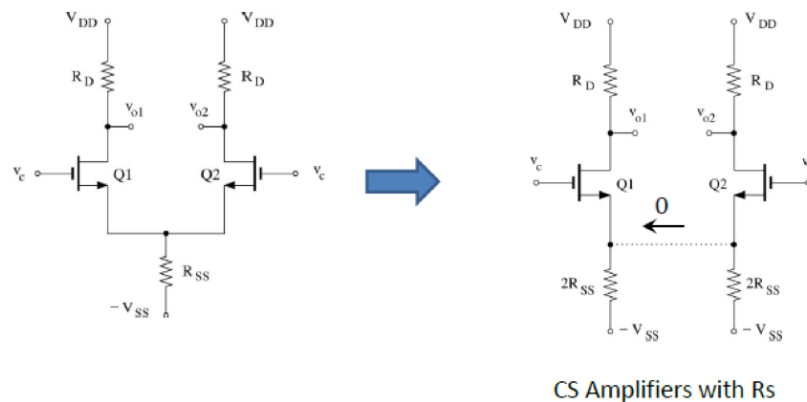- The common-mode circuit breaks into two identical half-circuits.



$$\frac{v_{o1}}{v_c} = \frac{v_{o2}}{v_c} = -\frac{g_m R_D}{1 + 2g_m R_{SS} + R_D/r_o}$$

Interaction of Common-Mode and Differential-Mode

$$A_{\text{cdm}} \triangleq \left. \frac{V_{\text{od}}}{V_{\text{ic}}} \right|_{V_{\text{id}}=0} \quad \text{and} \quad A_{\text{dcm}} \triangleq \left. \frac{V_{\text{oc}}}{V_{\text{id}}} \right|_{V_{\text{ic}}=0}$$

- In a perfectly balanced (symmetric) circuit, $A_{\text{cdm}} = A_{\text{dcm}} = 0$
- In practice, A_{cdm} and A_{dcm} are not zero because of component mismatch
- A_{cdm} is important because it indicates the extent to which a common-mode input will corrupt the differential output (which contains the actual signal information)

$$A_{\text{dm}} = \left. \frac{V_{\text{od}}}{V_{\text{id}}} \right|_{V_{\text{ic}}=0} = -g_m R_{\text{D}}$$

$$A_{\text{cm}} \simeq -\frac{g_m R_{\text{D}}}{1 + g_m (2R_{\text{TAIL}})} = -\frac{g_m R_{\text{D}}}{1 + 2g_m R_{\text{TAIL}}}$$

R_{SS}

$$\text{CMRR} \equiv \left| \frac{A_{\text{dm}}}{A_{\text{cm}}} \right| \Rightarrow \text{CMRR} = 1 + 2g_m R_{\text{TAIL}}$$

R_{SS}


52

CMRR should be as large as possible.


→ CMG should be minimized as much as possible to increase Noise Immunity.

Differential Pair Noise Immunity

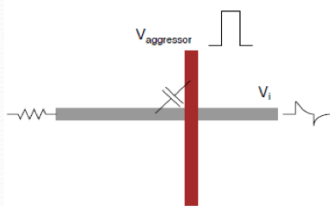- Differential signaling is immune to environmental noise.
- Any signal that affects both V_{in} and V_{ip} in the same way, will be ideally eliminated by the differential pair.



Single-ended signaling

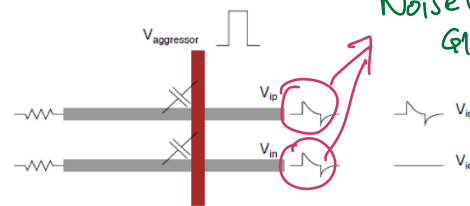


Differential signaling

Noise (or Glitch) because of capacitive coupling

- Similar argument is applicable to other kinds of interference such as ground bounce, and supply variation.
- Mismatch between the two half-circuits, limit the achievable noise immunity.

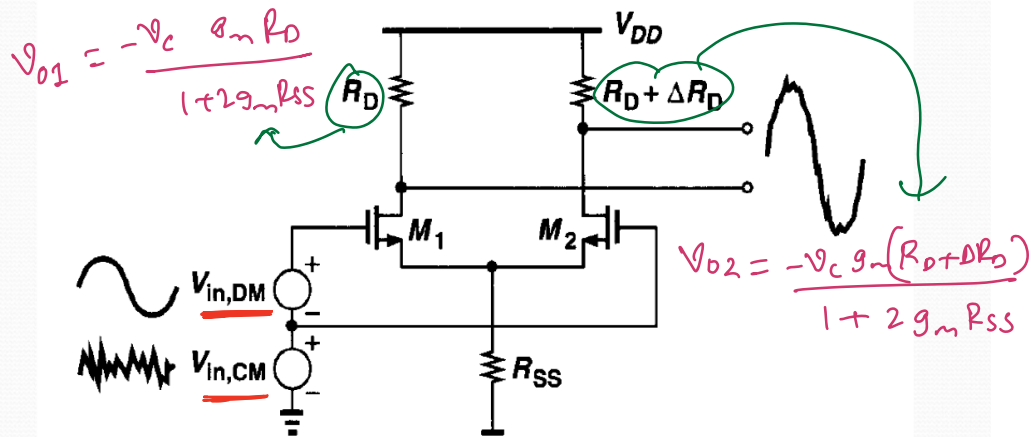Effect of CM noise in the presence of resistor mismatch




→ In practice even Resistor mismatch will because of manufacturing variations,
 → non-ideal conditions also effect the Noise

with perfect matching $V_{O2} - V_{O1} = 0$ immunity


with imperfect matching $V_{O2} - V_{O1} \neq 0$

→ This is fundamental issue we have in any practice realization of circuits.

Input Offset Voltage

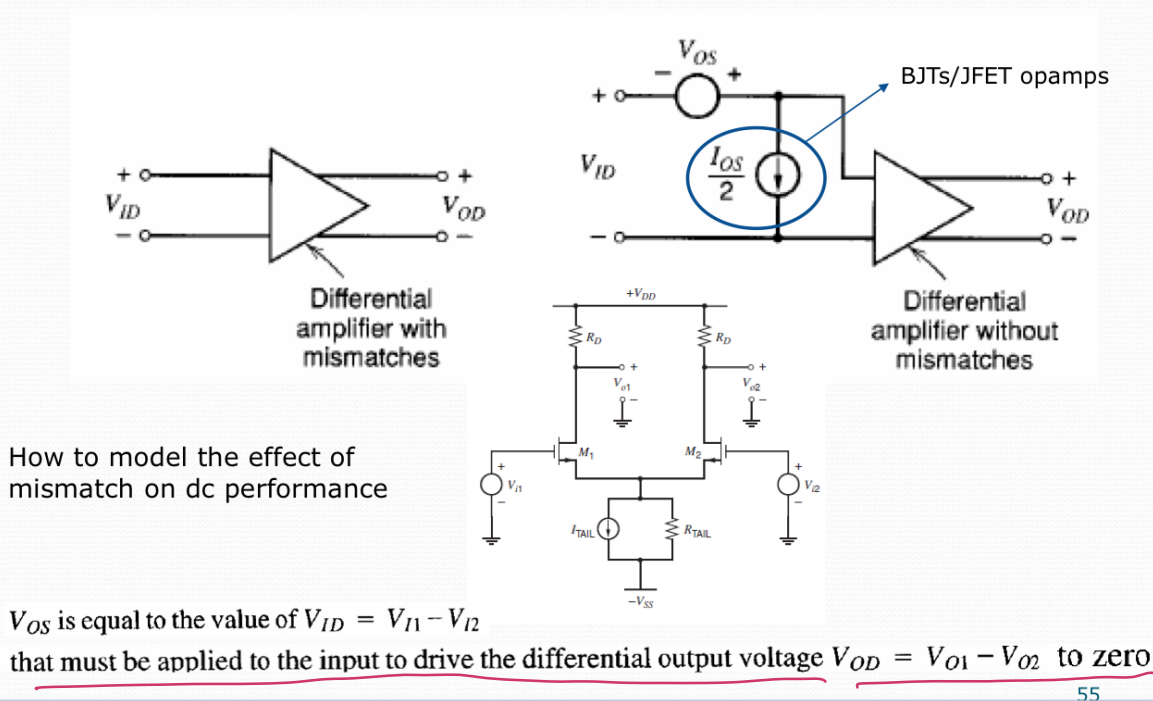

Input Offset-Voltage: MOSFET Pair

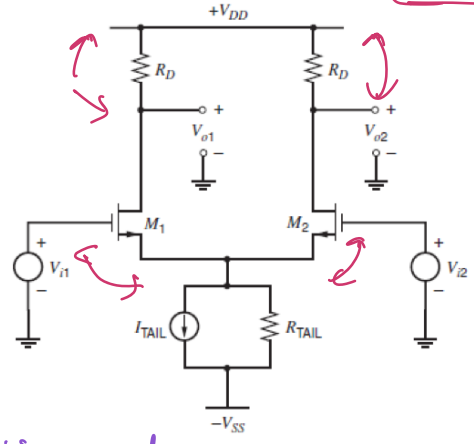

$$V_{ID} - V_{GS1} + V_{GS2} = 0 \quad V_{ID} = V_{GS1} - V_{GS2}$$

$$= V_{i1} + \sqrt{\frac{2I_{D1}}{k'(W/L)_1}} - V_{i2} - \sqrt{\frac{2I_{D2}}{k'(W/L)_2}}$$

For V_{OD} to be zero, $I_{D1}R_{D1} = I_{D2}R_{D2}$

What could go wrong...

① $\Delta V_t = V_{t1} - V_{t2}$
 $V_t = \frac{V_{t1} + V_{t2}}{2}$

② $\Delta(W/L) = (W/L)_1 - (W/L)_2$
 $(W/L) = \frac{(W/L)_1 + (W/L)_2}{2}$

③ $\Delta R_L = R_{L1} - R_{L2}$
 $R_L = \frac{R_{L1} + R_{L2}}{2}$

Definitions used below

$$\Delta I_D = I_{D1} - I_{D2}$$

$$I_D = \frac{I_{D1} + I_{D2}}{2}$$

$$I_{D1} = I_D + \frac{\Delta I_D}{2}$$

$$(W/L)_1 = (W/L) + \frac{\Delta(W/L)}{2}$$

$$I_{D2} = I_D - \frac{\Delta I_D}{2}$$

$$(W/L)_2 = (W/L) - \frac{\Delta(W/L)}{2}$$

56

→ $V_{ID} = V_{GS1} - V_{GS2}$ input difference voltage
 is equal to the difference
 b/w V_{GS1} & V_{GS2}

we should find what should be the values
 of V_{GS1} & V_{GS2} so that

$$I_{D1}R_{D1} = I_{D2}R_{D2}$$

because this is the condition that should be
 satisfied for the $V_{O1} = V_{O2}$

~~~~ What could go wrong...

- ① $\Delta V_t = V_{t1} - V_{t2}$
 $V_t = \frac{V_{t1} + V_{t2}}{2}$
- ② $\Delta(W/L) = (W/L)_1 - (W/L)_2$
 $(W/L) = \frac{(W/L)_1 + (W/L)_2}{2}$
- ③ $\Delta R_L = R_{L1} - R_{L2}$
 $R_L = \frac{R_{L1} + R_{L2}}{2}$

① Threshold differences b/w two transistors M_1 & M_2

② w/L Ratio difference b/w M_1 & M_2

③ Resistance difference in loads R_{L1} & R_{L2}

Q2 What are the implications of these variations?

$V_{G1} - V_{G2}$

$$V_{OS} = V_{t1} - V_{t2} + \sqrt{\frac{2I_{D1}}{k'(W/L)_1}} - \sqrt{\frac{2I_{D2}}{k'(W/L)_2}} \quad (=V_{ID})$$

$$= \Delta V_t + \sqrt{\frac{2(I_D + \Delta I_D/2)}{k'[(W/L) + \Delta(W/L)/2]}} - \sqrt{\frac{2(I_D - \Delta I_D/2)}{k'[(W/L) - \Delta(W/L)/2]}}$$

$$= \Delta V_t + (V_{GS} - V_t) \left(\sqrt{\frac{1 + \Delta I_D/2I_D}{1 + \frac{\Delta(W/L)}{2(W/L)}}} - \sqrt{\frac{1 - \Delta I_D/2I_D}{1 - \frac{\Delta(W/L)}{2(W/L)}}} \right)$$

This switching is discussed below

$$\simeq \Delta V_t + \frac{(V_{GS} - V_t)}{2} \left(\frac{1 + \Delta I_D/2I_D}{1 + \frac{\Delta(W/L)}{2(W/L)}} - \frac{1 - \Delta I_D/2I_D}{1 - \frac{\Delta(W/L)}{2(W/L)}} \right) \simeq \Delta V_t + \frac{(V_{GS} - V_t)}{2} \left(\frac{\Delta I_D}{I_D} - \frac{\Delta(W/L)}{(W/L)} \right)$$

$I_{D1}R_{L1} = I_{D2}R_{L2} \Rightarrow \frac{\Delta I_D}{I_D} = -\frac{\Delta R_L}{R_L}$

$V_{OD}=0$

GM

$$V_{OS} = \Delta V_t + \frac{(V_{GS} - V_t)}{2} \left(-\frac{\Delta R_L}{R_L} - \frac{\Delta(W/L)}{(W/L)} \right)$$

57

differential pair -offset

mercoledì 17 marzo 2021 11:40



$$\sqrt{\frac{2(I_D + \frac{\Delta I_D}{2})}{\beta'(\frac{W}{L} + \frac{\Delta W}{2})}} = \sqrt{\frac{2I_D \cdot (1 + \frac{\Delta I_D}{I_D \cdot 2})}{\beta' \frac{W}{L} (1 + \frac{\Delta W}{2 \cdot \frac{W}{L}})}} = \underbrace{\sqrt{\frac{2I_D}{\beta' \frac{W}{L}}}}_{V_{OV} = V_{GS} - V_T} \cdot \frac{\sqrt{1 + \frac{\Delta I_D}{2I_D}}}{\sqrt{1 + \frac{\Delta W}{\frac{W}{L} \cdot 2}}} = \text{Non Linear}$$

Taylor

$$\sqrt{1+x} \approx 1 + \frac{x}{2}$$

$k \cdot 1 \rightarrow x$

$$\sqrt{k} \approx \frac{k+1}{2}$$

(if $k \approx 1$)

$$k = \frac{(1 + \frac{\Delta I_D}{2I_D})}{(1 + \frac{\Delta W}{\frac{W}{L} \cdot 2})}$$

$$= V_{OV} \cdot \left[\frac{1 + \frac{\Delta I_D}{2I_D}}{1 + \frac{\Delta W}{\frac{W}{L} \cdot 2}} + 1 \right]$$

Linear

we convert Non-linear to Linear to analyze statistical properties of the behaviour.



$$\left(\frac{1 + \frac{\Delta I_D}{2I_D}}{1 + \frac{\Delta W}{\frac{W}{L}}} - \frac{1 - \frac{\Delta I_D}{2I_D}}{1 - \frac{\Delta W}{\frac{W}{L}}} \right) = \frac{(1 + \frac{\Delta I_D}{2I_D})(1 - \frac{\Delta W}{\frac{W}{L}}) - (1 - \frac{\Delta I_D}{2I_D})(1 + \frac{\Delta W}{\frac{W}{L}})}{1 - (\frac{\Delta W}{\frac{W}{L}})^2}$$

$$= \frac{\Delta I_D}{2I_D} + \frac{\Delta I_D}{2I_D} - \frac{\Delta W}{\frac{W}{L}} - \frac{\Delta W}{\frac{W}{L}} = \left[\frac{\Delta I_D}{I_D} - \frac{\Delta W}{\frac{W}{L}} \right]$$

when $V_{OD} = 0$

$$\star I_{D1} \cdot R_{L1} = I_{D2} \cdot R_{L2}, \quad V_{O1} = V_{O2}$$

% Variation of current - % Variation of gain factor

$$\left(I_D + \frac{\Delta I_D}{2} \right) \left(R + \frac{\Delta R}{2} \right) = \left(I_D - \frac{\Delta I_D}{2} \right) \left(R - \frac{\Delta R}{2} \right)$$

$$\cancel{I_D \cdot R} + \frac{\Delta I_D}{2} \cdot R + \frac{\Delta R}{2} \cdot I_D = \cancel{I_D \cdot R} - \frac{\Delta R}{2} \cdot I_D - \frac{\Delta I_D}{2} \cdot R \Rightarrow \Delta I_D \cdot R = -\Delta R \cdot I_D$$

$$\frac{\Delta I_D}{I_D} = -\frac{\Delta R}{R}$$

% variations of current = - % variations in resistance

~~***~~

controllable

$$V_{OS} = \Delta V_t + \frac{(V_{GS} - V_t)}{2} \left(-\frac{\Delta R_L}{R_L} - \frac{\Delta(W/L)}{(W/L)} \right)$$

undesired
offset
voltage difference

overdrive

uncontrollable

→ All these are inherent to manufacturing as designers we cannot control Intrinsic manufacturing variations.

→ But we can statistically Analyze these variations in Threshold, Resistance and Form factor

→ But what is under Designer's control is overdrive voltage

Revanth Reddy Pannala
EBIT, Unibo